
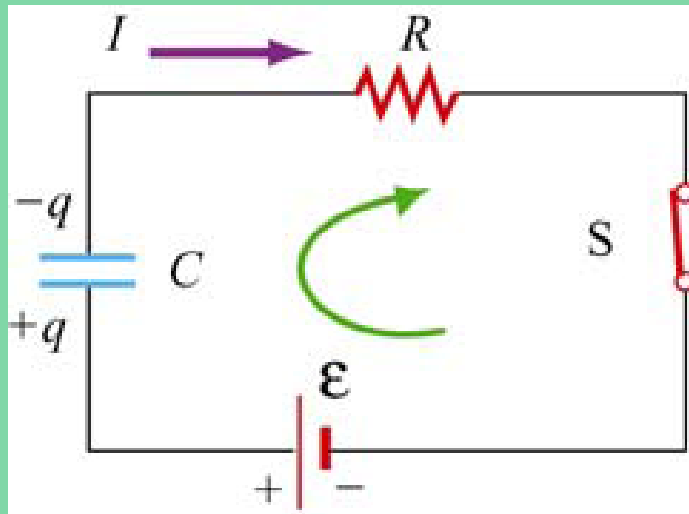


Circuito RC – Carga de un condensador

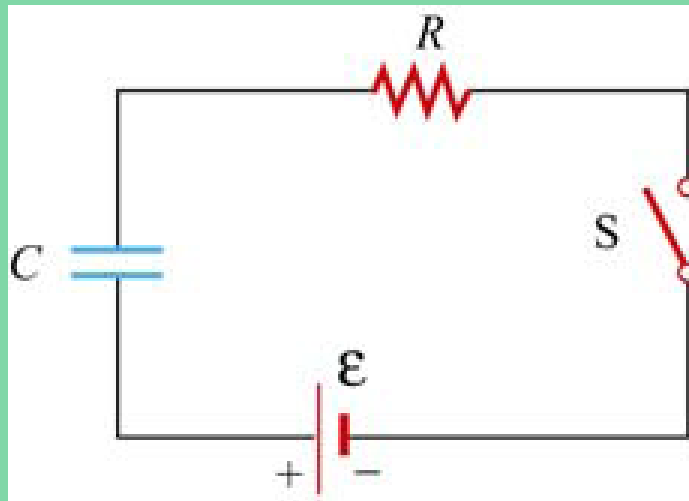

$$I(t)R = \varepsilon - V_C(t)$$


$$\begin{aligned} 0 &= \varepsilon - I(t)R - V_C(t) \\ &= \varepsilon - \frac{dq}{dt}R - \frac{q}{C} \end{aligned}$$

$$\frac{dq}{dt} = \frac{1}{R} \left(\varepsilon - \frac{q}{C} \right)$$

$$\frac{dq}{\left(\varepsilon - \frac{q}{C}\right)} = \frac{1}{R} dt \quad \Rightarrow \quad \frac{dq}{q - C\varepsilon} = -\frac{1}{RC} dt$$

$$\int_0^q \frac{dq'}{q' - C\varepsilon} = -\frac{1}{RC} \int_0^t dt'$$
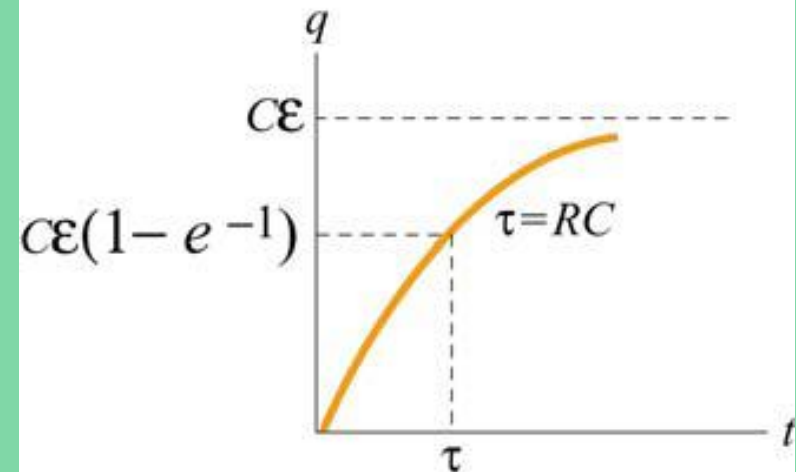
$$\ln\left(\frac{q - C\varepsilon}{-C\varepsilon}\right) = -\frac{t}{RC}$$





$$q(t) = C\varepsilon\left(1 - e^{-t/RC}\right) = Q\left(1 - e^{-t/RC}\right)$$

$$V_c(t) = \frac{q(t)}{C} = \varepsilon(1 - e^{-t/RC})$$


$$q(t = \infty) = C\varepsilon = Q$$

$$V_c = \frac{q(t = \infty)}{C} = \frac{Q}{C} = \varepsilon$$
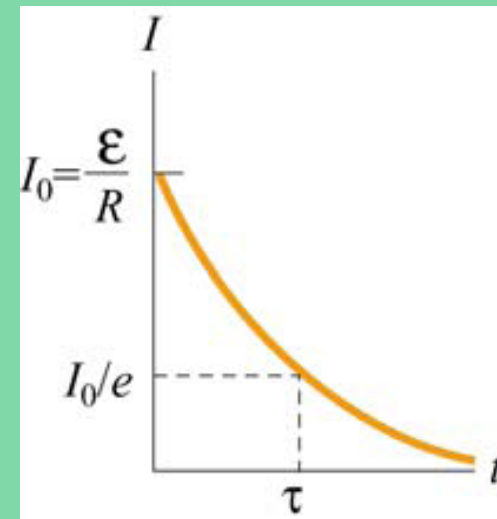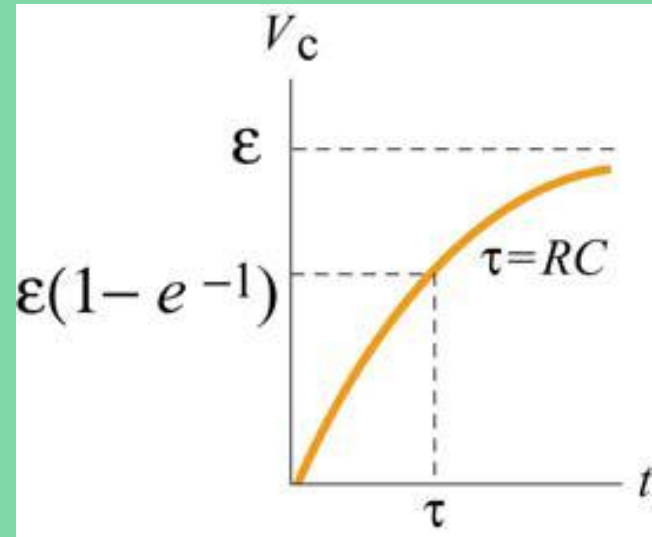
$$I(t) = \frac{dq}{dt} = \left(\frac{\varepsilon}{R}\right)e^{-t/RC} = I_0 e^{-t/RC}$$




Circuito RC – Descarga de un condensador

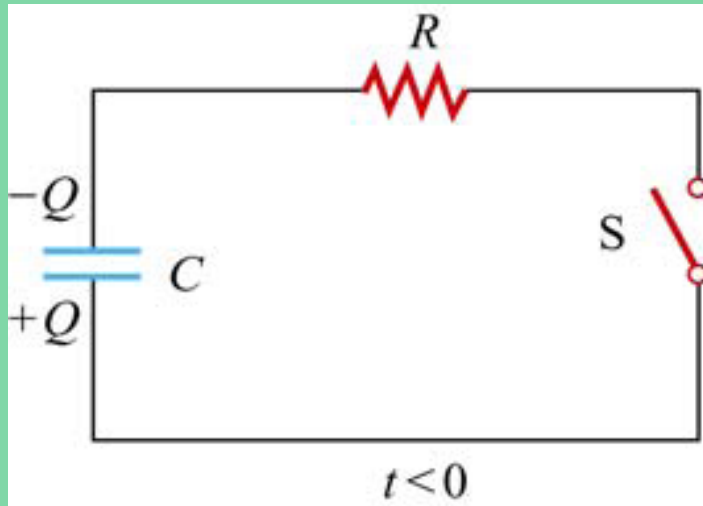

$$\frac{q}{C} - IR = 0$$

$$I = -\frac{dq}{dt}$$

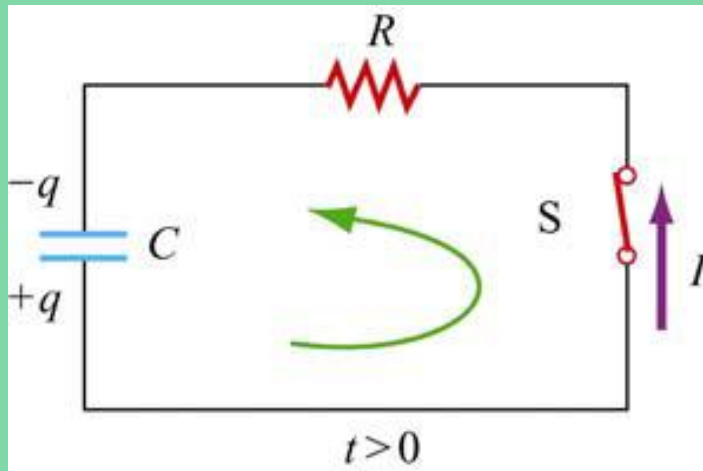


$$\frac{q}{C} + R\frac{dq}{dt} = 0$$

$$\frac{dq}{q} = -\frac{1}{RC}dt$$

$$\int_Q^q \frac{dq'}{q'} = -\frac{1}{RC} \int_0^t dt' \quad \Rightarrow \quad \ln\left(\frac{q}{Q}\right) = -\frac{t}{RC}$$

$$q(t) = Q e^{-t/RC}$$
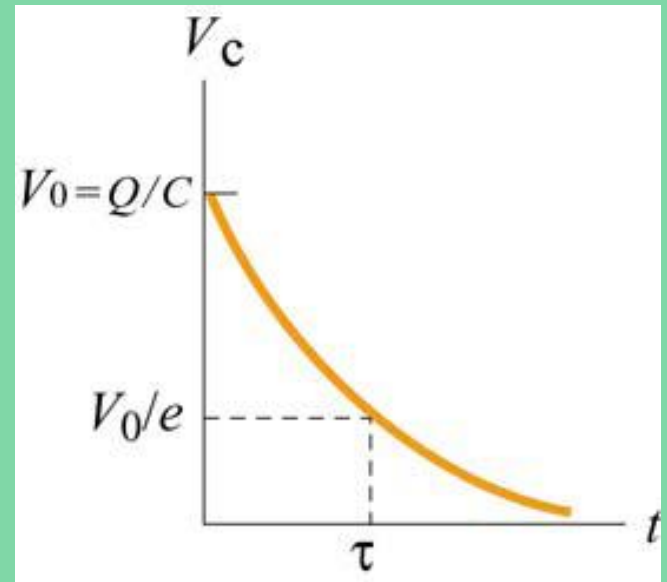
$$V_c(t) = \frac{q(t)}{C} = \left(\frac{Q}{C}\right) e^{-t/RC}$$



$$I = -\frac{dq}{dt} = \left(\frac{Q}{RC} \right) e^{-t/RC}$$

